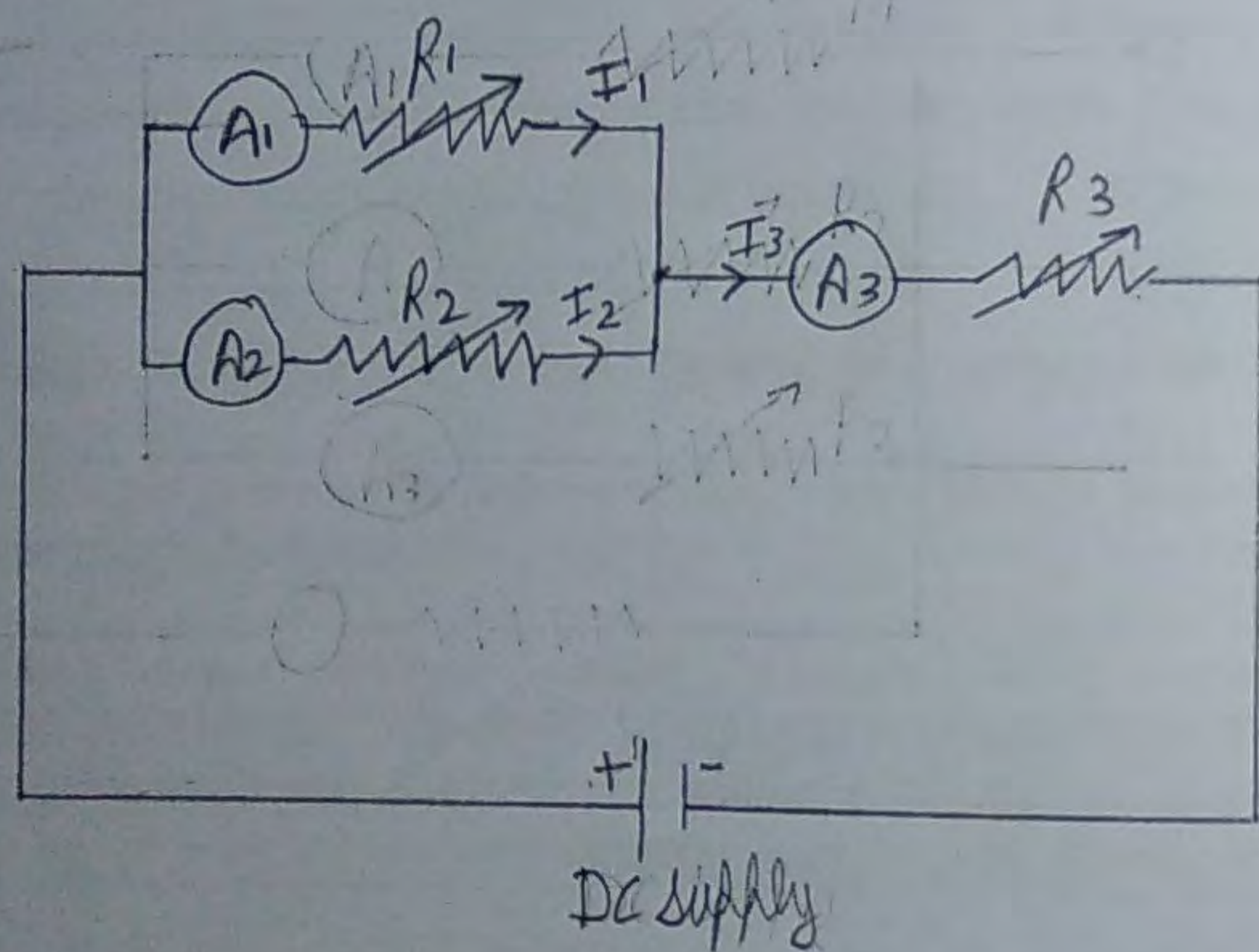


figure-1



Circuit Diagram

Experiment-1

Aim: To verify Kirchhoff's current law.

Apparatus Required: Ammeter, Rheostat, D.C. supply, connecting wires.

Theory: It states that the algebraic sum of currents meeting at a junction of conductors is zero.

In other words, the sum of currents flowing away from a junction is equal to the sum of current flowing towards the junction.

In fig-1, I_1, I_2, I_3 & I_4 currents are meeting at a junction.

$$I_1 + I_2 = I_3 + I_4 \quad \text{or} \quad I_1 + I_2 - I_3 - I_4 = 0 \quad (\text{figure-1})$$

Observation Table.

S.No.	I_1 (A)	I_2 (A)	I_3 ($I_1 + I_2 = I_3$) (A)
1.	17	4.6	21.6
2.	16.4	5.1	21.5
3.	21.7	6.3	28

Teacher's Signature : _____

Calculations.

On adding the reading from A_1 & A_2 ; we get it equal to the reading of A_3 .


$$I_1 + I_2 = I_3 \quad \text{or} \quad I_1 + I_2 - I_3 = 0.$$

Result.

Kirchhoff's Current law is verified, since the ~~at~~ algebraic sum of currents at junction is equal to zero.

Precautions:

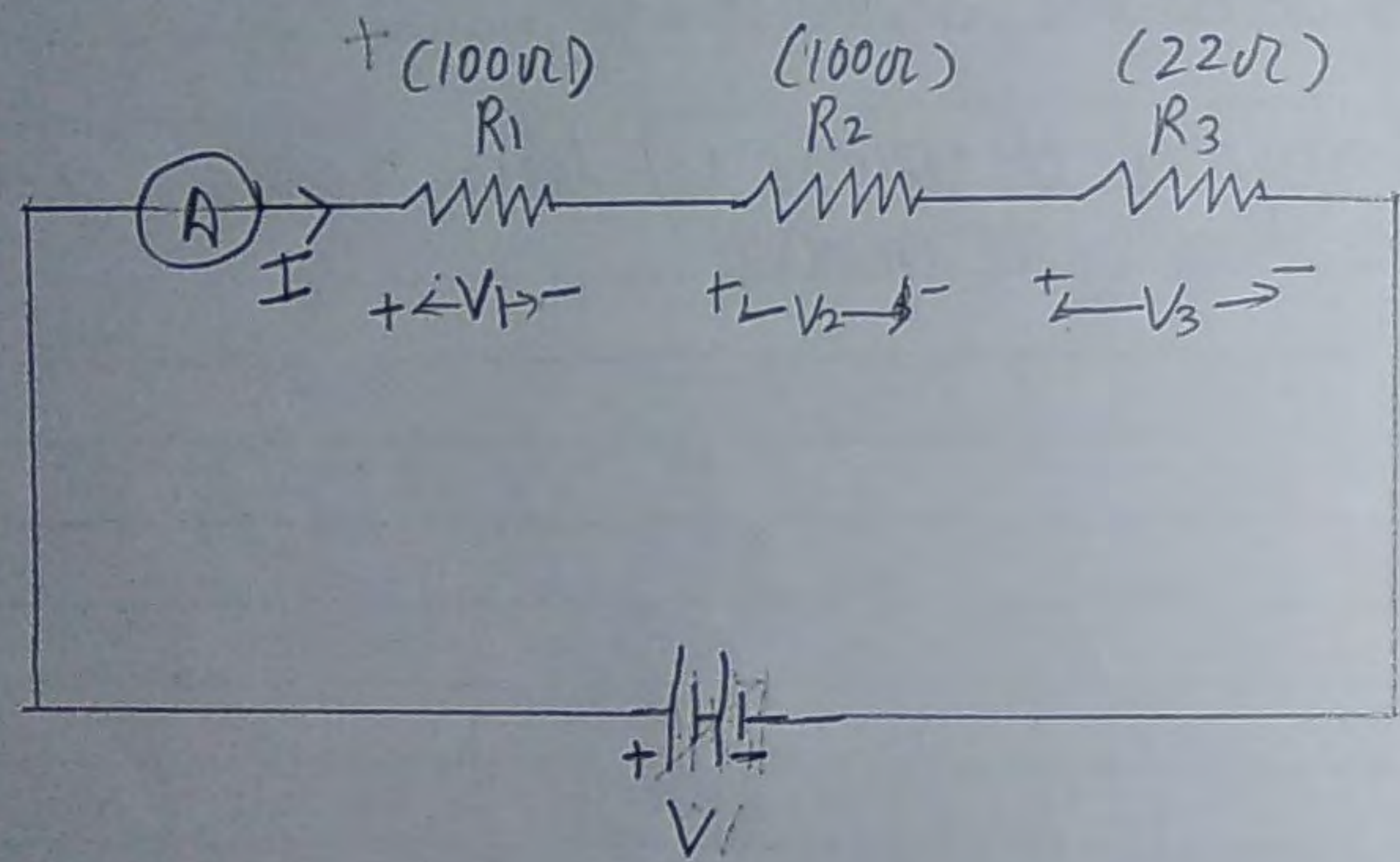- (i) All the connections should be tight.
- (ii) Before operating the circuit, and taking readings, check the zero reading of the ammeter.



Circuit diagram

Experiment-2

Aim: To verify Kirchhoff's Voltage Law.

Apparatus Required: Voltmeter, ~~Ammeter~~ ^{Ammeter}, Resistors, D.C. Power Supply, ^(variable)

Theory: According to this law, ⁶⁶the algebraic sum of voltage around a close loop is zero⁷⁷.

It can be also stated as ⁶⁶In any closed circuit, the algebraic sum of the products of current and Resistance in each of the conductor is equal to the algebraic sum of emf of the batteries.

Observation Table:

S.No.	V_{cell}	I (mA)	V_1 (mA)	V_2	V_3	$V_1 + V_2 + V_3$
1	10V	60 mA	5.81V	2.91V	1.28V	10V
2	12V	70 mA	6.98V	3.49V	1.53V	12V
3	15V	90 mA	8.72V	4.36V	1.92V	15V

Calculations:-

Add the Voltage V_1, V_2 & V_3 recorded from first, second & third volt meter, record the same in the last column of this table.

Result:

As the voltage V and $V_1 + V_2 + V_3$ are equal, i.e.

$$V = V_1 + V_2 + V_3.$$

Krichhoff Voltage law is verified.

Precautions.

- (i) All connections should be tight.
- (ii) Before connecting the instrument, check their zero reading.

Experiment - 3.

Aim: To Find out efficiency of single phase transformer :

Apparatus Required: Single phase transformer, Auto transformer, Wattmeter, Ammeter, Voltmeter, Connecting Wires.

Theory: On a practical transformer there are two types of losses

1. Copper loss

2. Iron loss

Therefore output of transformer is always less than the input of transformer.

~~Here transformer is loaded with variable resistance load. Input to the transformer can be formed out by using attachment and help of voltmeter and ammeter.~~

$$\text{Efficiency of transformer} = \left(\frac{\text{output power}}{\text{Input power} + \text{losses}} \right) \times 100\%$$

$$= \frac{V_2 I_2}{\text{Input power} + \text{losses}} \times 100\%$$

Observation Table.

	Rated Voltage	Rated current	Losses
Open circuit	230	4.34	$45 \times 2 = 90$
closed circuit	230	4.34	$1.5 \times 4 = 6 \text{ watt}$

Total losses = 96 watt

Total losses = 96 watt

Calculations $\eta =$

$$\text{Efficiency, } \eta = \left(\frac{\text{Output power}}{\text{Input power} + \text{losses}} \right) \times 100\%$$

$$\approx \frac{1000}{1000 + 96}$$

$$\eta = \left(\frac{1000}{1000 + 96} \right) \times 100 = 91.24\%$$

Result

Efficiency of the transformer is 91.24%.

Precautions

Avoid loose connections.

Experiment - 4.

Aim: Starting method of 3-phase induction motor by star-delta.

Apparatus: Three phase induction motor starter with panel, operating wire, A.C. supply.

Theory: A three phase motor gives three times power output when the starter winding are connected in delta. If connected in star, but will take $\frac{1}{\sqrt{3}}$ of the current from the supply when connected in delta. The starting torque depend in star is $\frac{1}{3}$ that times than in delta.

- A two position switch (Manual and automatic) is provided through a timing.
- Starting in star reduce the starting current.
- When motor has accelerated up to speed, and current is reduced to its normal value the starter is moved to run position with the winding now connected in delta.
- More complicated than the DC starter a motor with a star-delta starter may not produce sufficient torque to start against full load. So output is reduced in start position, thus the motor are started under a light load.

Experiment-5.

Aim: Characteristic of DC compound generator.

Apparatus: Three phase Induction motor, D.C. supply load (ball), connecting wire, panel.

Theory: In compound wound DC generator both the field winding are combined (series and shunt) either. This type of generator can be used as either long shunt or short shunt compound wound generator.

In both the cases the external characteristics of generator will be nearly same as the compound wound generator are very rarely used. Electric current in series field also produces more flux and compensate the drop in the voltage, and do operate machine at constant voltage.

The combination of series generator and a shunt generator give the characteristics which are required.

The voltage drop in shunt machine is therefore compensated by the voltage rise in series motor.

Observation Table

S. No.	Current	Voltage	load
1	0	270	0
2	1	280	200
3	1.8	267	400

Precaution:

- Avoid loose wires, cables and connectors
- Don't wear loose clothes.

Experiment - 6

Aim: External characteristic of DC shunt generator.

Apparatus: Shunt generator, panel with starter, DC motor, load connecting wire.

Theory: The external characteristic of a shunt generator is the relation between terminal voltage V and load current I .

$$V = E - I_a R_a$$

$$= E - (I_L + I_{sh}) R_a$$

When external characteristic curve under internal characteristic curve, terminal voltage will properly be maintained constant by adjusting field resistor automatically.

Observation Table:

S.No.	Current	Voltage	Load (watt) PUL
1	0	280	0
2	0.6	270	100
3	1	260	200

Teacher's Signature: _____

Precautions

- 1.) Avoid loose wires, cables and connections.
- 2.) Don't wear loose clothes.