

Electrical Engineering in India


Introduction: - Electrical Engineering began at the end of 19th century

- * Power Supply Start in "Darjaling" at 1897
- * Start Shivasamudra Hydro plant in 1902 in Karnataka
- * Total Capacity of Electrical Power =
1,18,419 MW (2002-03)
2,74,818 MW (2015)
1400 MW (1947)
- * Total Capacity of Electrical Power in UP = 4120 MW
- * Per person Electrical power = 130 kWh (2012-13)
- * There is 1.25 Crore villages, where is not Electric Supply
- * Nuclear Power in India = 4120 MW
- * Electric Track of Railway = 17500 km (31 March 2015)
- * Total Reactor in India = 14

Min. M. T. ...
Power Supply ...

1.5 Molecules

(2)

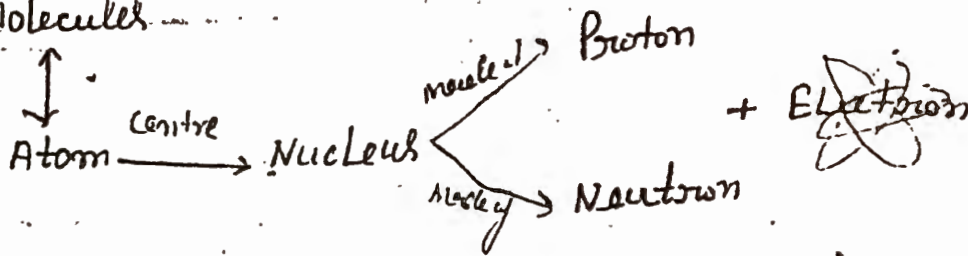

Potter

Combination of similar Atom \rightarrow Element

" " dissimilar " \rightarrow Compound

Total No. of element - 106

Compound $\rightarrow \infty$

Current: \rightarrow Transfer of charge from one point to other is termed as Electric Current.



Net motion of Electron

1 electron charge $\rightarrow 1.6021 \times 10^{-19}$ Coulomb

1.6021×10^{-19} Coulomb charge - have - 1 electron

$$\frac{1}{1.6021 \times 10^{-19}}$$

$$= 6.24 \times 10^{18}$$

Time rate of flow of free electrons

$$\text{Current } I(t) = \frac{dq(t)}{dt} = \frac{\text{Coulomb}}{\text{Second}} = \text{Ampere (A)}$$

Termed in honour of the French Physicist

Andre Marie Ampere (1775 - 1836)

French word intensite = Current

M. Ind. Murtaza

Voltage / Potential difference: → Time derivative of the flux ϕ

$$V(t) = \frac{d}{dt} \phi(t) = \frac{\text{Weber}}{\text{Second}} = \text{Volts (V)}$$

Termed in honour of Italian Physicist Alessandro Volta (1745-1827)

* Power: - Product of instantaneous value of voltage and current
 $P(t) = V(t) i(t) = \text{Power} \Rightarrow \text{Watt}$


British Inventor James watt (1738-1819)

* Energy Delivered: -

$$E(t_0 - t) = \int_{t_0}^t P(x) dx = \int_{t_0}^t V(x) i(x) dx = \text{Watt Second}$$

Joule

British Scientist J.P. Joule (1818-1869)

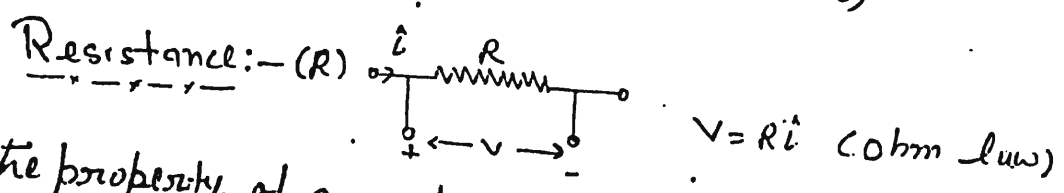

The property of a material which oppose the flow of electron is called resistance

George Simon Ohm (1787-1854). German mathematician

By experiment

$$R \propto \frac{l}{A} \equiv R = \rho \frac{l}{A}$$

ρ = specific resistance or resistivity

Conductance (G) = $\frac{1}{R}$

$$R = \rho \frac{l}{A}$$

$$G = \frac{1}{\rho} \frac{A}{l} = \sigma \frac{A}{l}$$

σ = Conductivity

A = Area of conductor
l = length of conductor


Temperature effect

$$R_t = R_0 (1 \pm \alpha t)$$

α = Temperature coefficient

Combination of Resistance:-

In Series:-

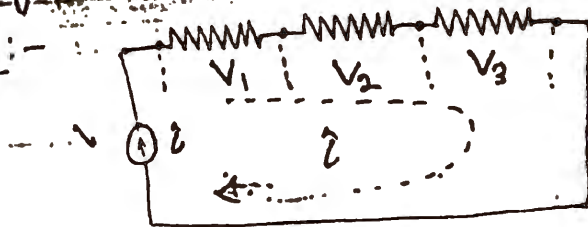


Current Same
Voltage difference

$$V = V_1 + V_2 + V_3 \quad V = IR$$

$$IR = IR_1 + IR_2 + IR_3$$

$$R = R_1 + R_2 + R_3$$

In Parallel:-

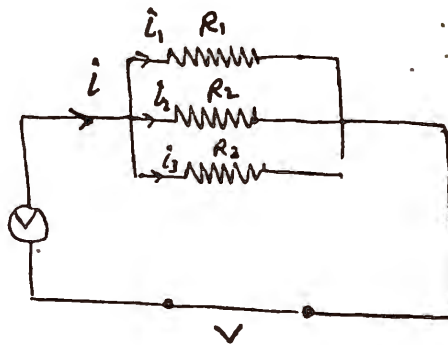

Voltage Same
Current different

$$I = I_1 + I_2 + I_3$$

$$\frac{V}{R} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

* Inductance (L): \rightarrow It is the property of the material (Conductor) by virtue of which it oppose the change in direction or magnitude of current.


$$L = \frac{N\phi}{I}$$

$$L = \frac{N\phi}{I}$$

N = Number of turns

ϕ = flux in weber.

I = Current

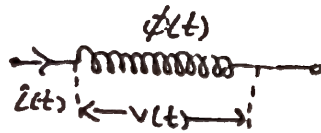

Current flow \rightarrow change in flux \rightarrow voltage induced

Scanned with OKEN Scanner

$$V = L \frac{di}{dt}$$

$$V = L \frac{di}{dt} \Rightarrow L = \frac{V}{\frac{di}{dt}} = \frac{V dt}{di} = \frac{d\phi}{di}$$

$$V = L \frac{di}{dt} = L \frac{d}{dt} (I_m \sin \omega t)$$

$$\Rightarrow L I_m \omega \cos \omega t = I_m \omega L \sin(\omega t + \pi/2)$$

$$V = \omega I_m L \sin(\omega t + \pi/2)$$

$$V = \omega L I_m \sin(\omega t + \pi/2)$$

$X_L =$ Inductive reactance in Ohm

$$V_m = X_L I_m$$

$$X_L = \omega L$$


By experiment $L = \frac{\mu_0 \mu_r N^2 A}{l} = \text{Henry}$ $\mu_0 \mu_r =$ Permeability

Combination of Inductance:-

In Series:- $L = L_1 + L_2 + L_3 + L_4 + \dots$

In Parallel:- $\frac{1}{L} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \frac{1}{L_4} + \dots$

Mutual Inductance

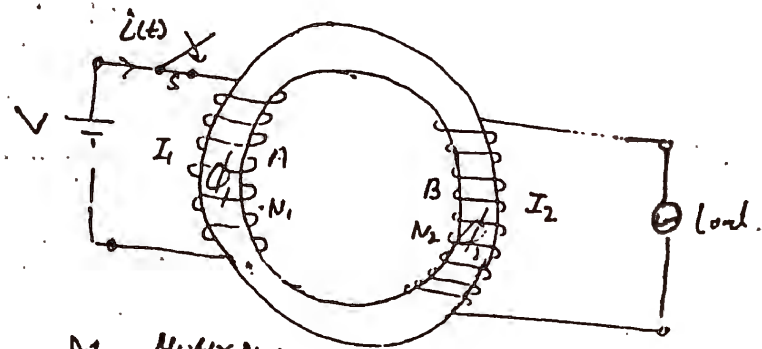

$$M = \frac{\mu_r \mu_0 N_1 N_2 A}{l}$$

$$M = k \sqrt{L_1 L_2}$$

$$M = \frac{N_1 N_2}{S}$$


$$M = k \sqrt{L_1 L_2}$$

S, Reluctance of the coil

$$\text{Energy Store} = \frac{1}{2} L I^2$$

Mohd. Muneer

Capacitance (C) :- Farad

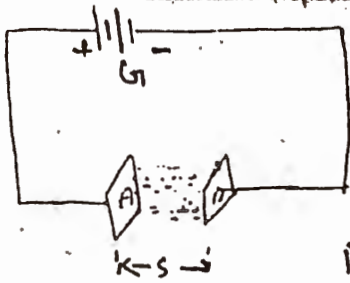

$$Q \propto V$$

$$Q = CV$$

$$C = \frac{Q}{V} \text{ Farad}$$

A.C. Through
Resistance only

in honour Michael Faraday
- the reciprocal of Capacitance is called Elastance

$$C = \frac{\epsilon_0 \epsilon_r A}{d} \text{ Farad}$$

dielectric

$$Q \propto V \Rightarrow Q = CV \Rightarrow C = \frac{Q}{V}$$

$$i = \frac{dq}{dt} = C \frac{dv}{dt} \Rightarrow i = C \left(\frac{dv}{dt} \right) \Rightarrow \int dv = \frac{1}{C} \int i dt$$

$$V(t) = \frac{1}{C} \int_0^t i(t) dt + \left(\frac{qv}{C} \right)$$

$$V = V_m \sin \omega t$$

$$i = C \left(\frac{dv}{dt} \right) = C \frac{d}{dt} (V_m \sin \omega t) = C V_m \omega \cos \omega t$$

$$i = I_m \sin(\omega t + \pi/2)$$

$$V_m = \frac{I_m}{\omega C} \quad \frac{I_m}{\omega C} = I_m X_C$$

$$X_C = \frac{1}{\omega C}$$

$$\text{Energy Store} = \frac{1}{2} CV^2$$

Mohd. Murtaza

A.C. Through Resistance, Inductance, Capacitance only:---

Resistance only: - $V = V_m \sin \theta = V_m \sin \omega t$ $V = IR$



$$V = IR$$

$$IR = V_m \sin \omega t$$

$$I = \frac{V_m}{R} \sin \omega t \Rightarrow \hat{i} = \frac{V_m}{R} \text{ where } \sin \omega t \text{ is unity}$$


$$\hat{I} = \frac{V_m}{R}$$

$$\hat{i} = I_m \sin \omega t$$

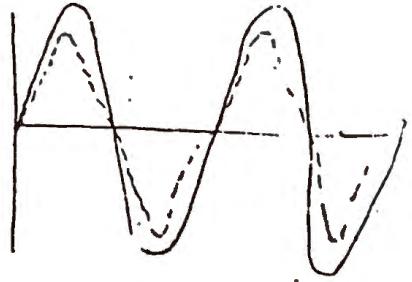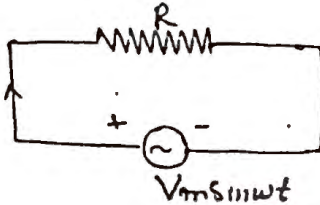

$\Rightarrow V$
 $\Rightarrow I$

Inductance only: ->

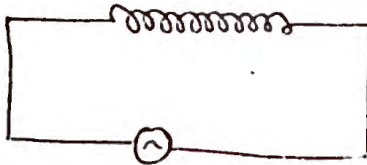

$$V = L \frac{di}{dt}$$

$$V = V_m \sin \omega t \dots \textcircled{1}$$

$$L \frac{di}{dt} = V_m \sin \omega t$$

$$\frac{di}{dt} = \frac{V_m}{L} \sin \omega t \, dt$$


Integrating on both side

$$i = \frac{V_m}{L} \int \sin \omega t \, dt$$

$$= \frac{V_m}{\omega L} (-\cos \omega t)$$

$$\hat{i} = \frac{V_m}{\omega L} \sin (\omega t - \pi/2)$$
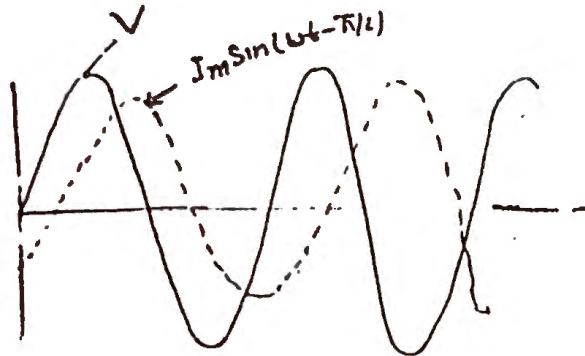
$$\hat{i} = I_m \sin (\omega t - \pi/2) \dots \textcircled{11}$$



Capacitance only:- it charged first in one direction and then in the opposite direction

$$q = CV$$

$$q = C V_m \sin \omega t$$

$$i = \frac{dq}{dt} = \frac{d}{dt} (C V_m \sin \omega t) = \omega C V_m \sin \omega t$$

$$i = \frac{V_m}{\frac{1}{\omega C}} \cos \omega t = \frac{V_m}{\frac{1}{\omega C}} \sin(\omega t + \pi/2)$$


$$I_m = \frac{V_m}{\frac{1}{\omega C}} = \omega C V_m$$

$$i = I_m \sin(\omega t + \pi/2)$$

$$X_c = \frac{1}{\omega C}$$

$$V = V_m \sin \omega t$$


$$i = I_m \sin(\omega t + \pi/2)$$

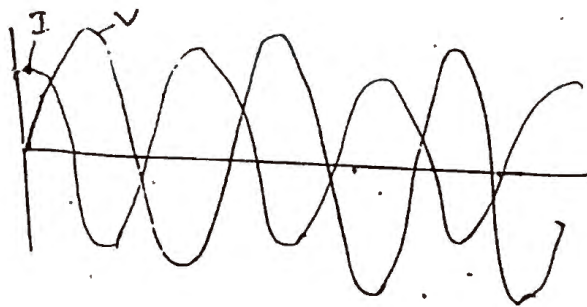

Applied Mathematics

A.C. Fundamentals:-

H

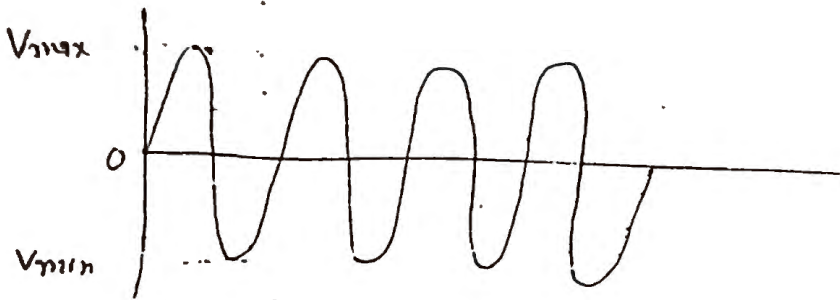

When a rectangular coil of area $A \text{ m}^2$ rotates in a flux density of B Tesla at an angular frequency (ω) rad/sec per second, therefore then the emf induced in that coil

$$e = \omega B A \sin \theta$$

if there are N turns then

$$e = \omega N B A \sin \theta$$

$$e = E_{\text{max}} \sin \theta$$

$$e = E_{\text{max}} \sin \omega t$$

For phase difference (ϕ)

$$i = I_{\text{max}} \sin (\omega t \pm \phi)$$

$$e = E_{\text{max}} \sin (\omega t \pm \phi)$$

R.M.S value
$$I_{\text{rms}} = \sqrt{\frac{I_1^2 + I_2^2 + I_3^2}{n}}$$

$$I_{\text{rms}} = \frac{I_0}{\sqrt{2}} \quad V_{\text{rms}} = \frac{V_0}{\sqrt{2}} \quad \begin{matrix} 220 \text{ volt} \\ 36 \text{ volt} \end{matrix}$$

Average value $I_{avg} = \frac{I_1 + I_2 + I_3 + \dots + I_n}{n}$

For Sinusoidal Current

$$I_{rms} = \frac{I_m}{\sqrt{2}}$$

$$I_{avg} = \frac{2I_m}{\pi}$$


* Frequency of voltage & current is same in A.C. current

Form factor = $\frac{\text{r.m.s. value}}{\text{Average Value}}$

Peak factor = $\frac{\text{Maximum Value}}{\text{r.m.s. Value}}$


Power = $V_{rms} \times I_{rms} = VI \cos \phi$

Phase difference: $\rightarrow \phi$

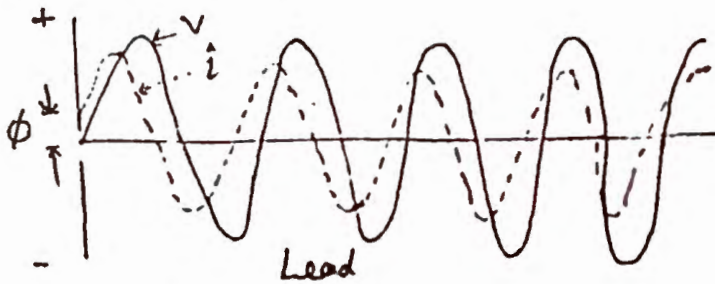

$$V = V_0 \sin \omega t$$

$$i = I_0 \sin(\omega t + \phi)$$

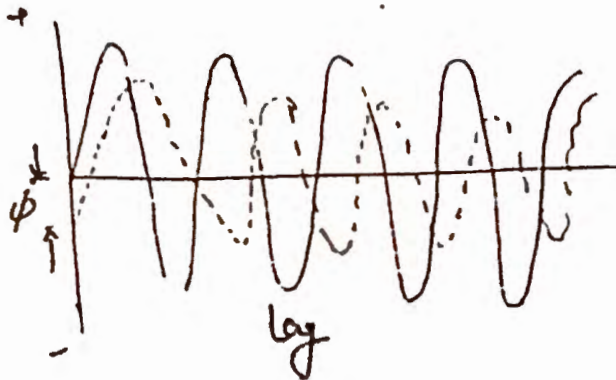


$$V = V_0 \sin \omega t$$




$$i = I_0 \sin(\omega t - \phi)$$

Mohd. Murtaza


Voltage Divider formula:-

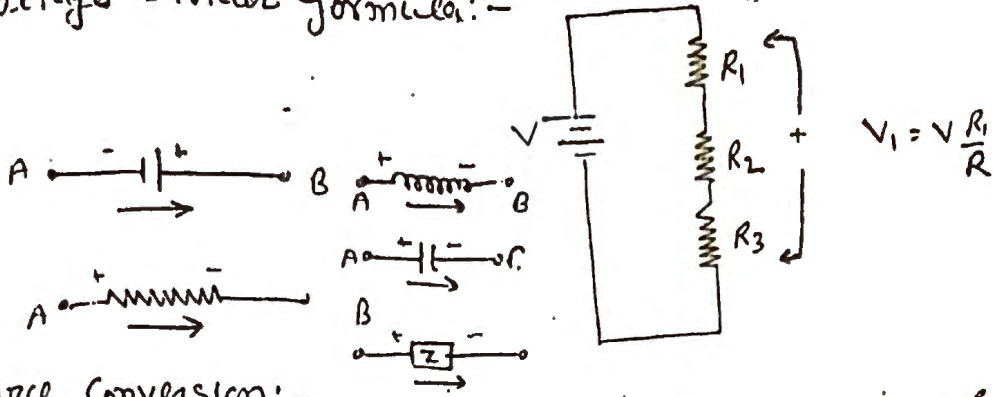


Source Conversion:-

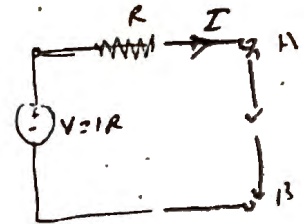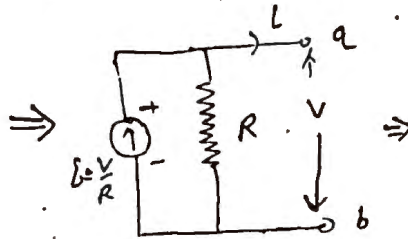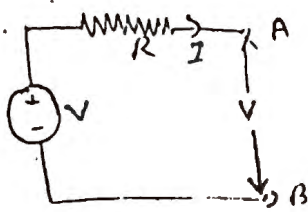

Independent Source

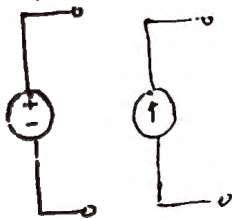

Dependent Source

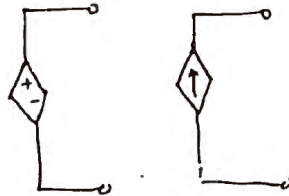

Absolute permeability $\mu = \frac{B}{H} = \frac{\text{Flux density}}{\text{Magnetising Force}}$

Relative permeability $\mu_r = \frac{\text{Flux density in the media}}{\text{Flux density in the vacuum}}$

Susceptibility (χ) = $\frac{I}{H}$

Reluctance:- Property of a material which opposes the creation of magnetic flux

Reluctance = $\frac{l}{\mu_0 \mu_r A} = \frac{l}{\mu A}$

Mohd. Mustafa


Network Theorem

Network Theorem are used for solving various network at save time and Considerably reduce the laborious Mathematical work.

Kirchhoff's laws:-

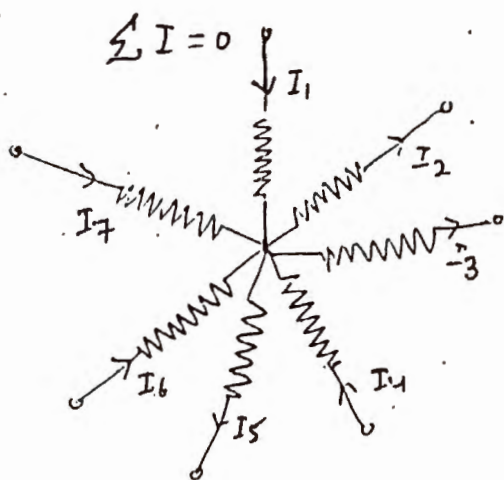(i) Kirchhoff's first law or Point law or Current law (KCL)

Statement:- The algebraic sum of the current meeting at a Point (or junction) is zero



$$\sum I = 0$$

$$I_1 + (-I_2) + (-I_3) - I_4 +$$


$$(-I_5) + I_6 + I_7 = 0$$

गो दूर गा रे ए (-)

(ii) Kirchhoff's Second law or Mesh law or Voltage law (KVL)

Statement:- The algebraic sum of all branch voltage around ~~and~~ any closed loop of a network is zero at all direction instant of it.

$$\sum V = 0$$

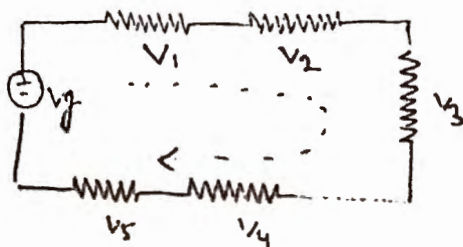

$$-V_g + V_1 + V_2 + V_3 + V_4 + V_5 = 0$$

clockwise direction

(1) Superposition Theorem:- The statement of Superposition Theorem is that


"The response in any element of linear, bilateral network containing more than one source is the sum of the response produced by the sources each acting independently"

it is applicable for those network which contain more than one voltage and current sources.

(2) Thevenin Theorem:- "Any two terminal network when viewed from its any two point can be replaced by a single voltage source in series with a single resistance".


The equivalent voltage source is designated by V_{th} and the equivalent resistance R_{th}

$$I = \frac{V_{th}}{R_L + R_{th}}$$

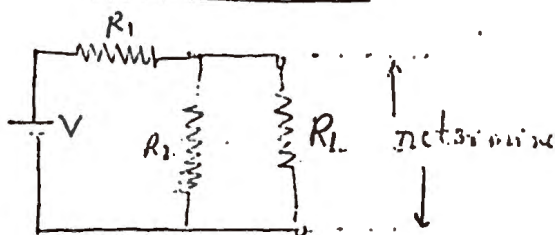

Dr. M. Marjazi

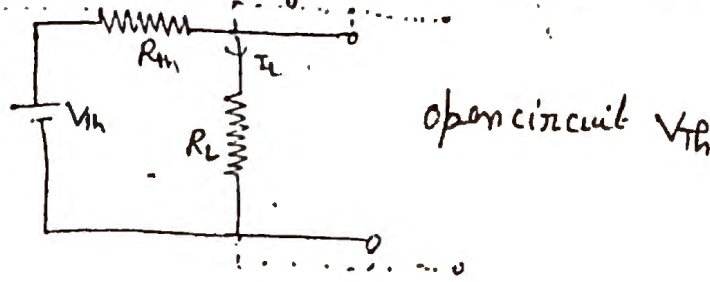Step 1: - Remove the R_L from the circuit & determine V_{th}



Step 2: → Determine the circuit current I


$$I = \frac{V}{R_1 + R_2}$$

$$V_{th} = \frac{V}{R_1 + R_2} \cdot R_2$$

Step 3: - Remove the battery from the circuit and determine the R_{th} from A and B

$$R_{th} = R_1 \parallel R_2 \Rightarrow \frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{R_1 + R_2}{R_1 R_2} \Rightarrow R = \frac{R_1 R_2}{R_1 + R_2}$$

Step 4: → Determine the current I

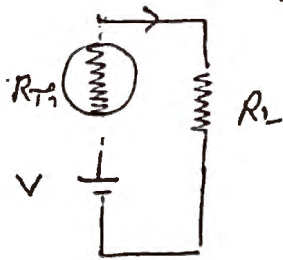

$$I = \frac{V_{th}}{R_{th} + R_L}$$



Handwritten calculations:

$$\frac{42}{12 \times 6} = \frac{42}{72} = \frac{7}{12}$$


$$\frac{42}{105} = \frac{2}{5}$$

$$\frac{14}{15} = \frac{14}{15}$$

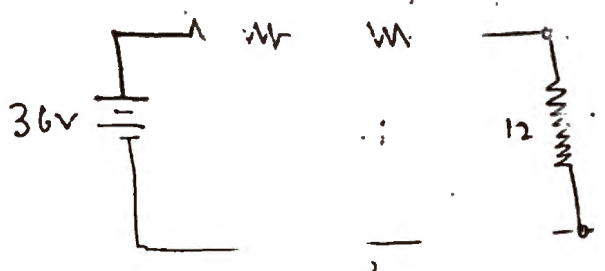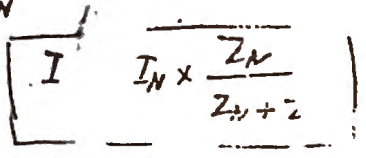Norton's theorem: \rightarrow Any two terminal linear network containing energy sources and impedance can be replaced by a simple two terminal network consisting of a single current I_N in parallel with impedance Z_N



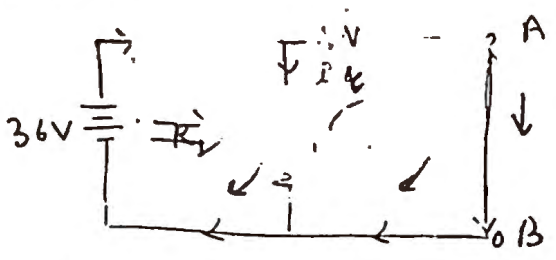Step 1:- Short circuit terminals a and b which the current is to be found.




$$\begin{aligned}
 -36 + 3I_1 + 6(I_1 - I_2) &= 0 \\
 4I_2 + 6(I_2 - I_1) &= 0 \\
 9I_1 - 6I_2 &= 36 \quad \text{--- (1)} \\
 -6I_1 + 10I_2 &= 0 \quad \text{--- (2)}
 \end{aligned}$$

$$\begin{aligned}
 R &= 3 + 4 \parallel 6 \\
 &= 3 + \frac{4 \times 6}{4 + 6} = 3 + \frac{24}{10} \\
 I &= \frac{36}{5.4} = \frac{20}{3} \text{ A}
 \end{aligned}$$


$$I_2 = 4$$

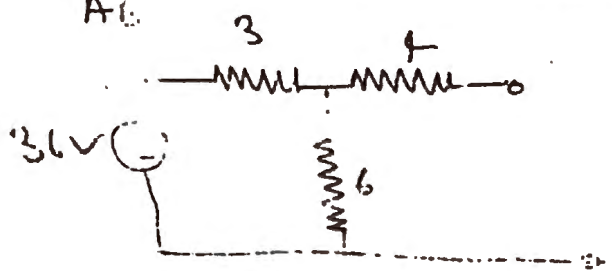Step 2:- Remove the short circuit terminals from a and b.



work
impedance

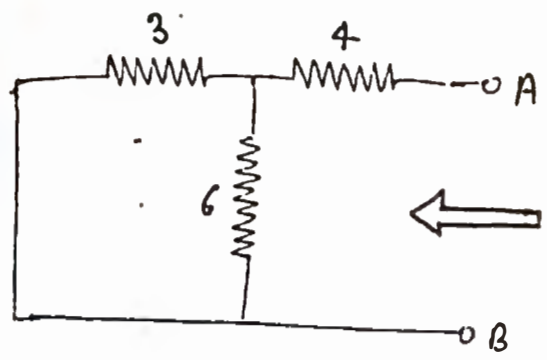3: - Remove the Battery and Determine R_N from




$$R_N = 4 + 3 // 6 = 4 + \frac{3 \times 6}{3 + 6} = 4 + \frac{18}{9} = 4 + 2 = 6 \Omega$$

Step 4:- Determine I from formula

$$I = I_N \cdot \frac{Z_N}{Z_N + Z_L} = 4 \cdot \frac{6}{6 + 12} = \frac{24}{18} = 1.33 \text{ A}$$

Maximum Power Transfer Theorem:- The statement is as

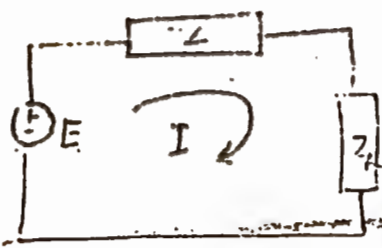Maximum power will be delivered by a network to an impedance Z_R if the impedance of Z_R is the complex conjugate of the impedance Z of the network, measured looking back into the terminal of the network.



$$I = \frac{E}{Z + Z_R} \quad (P = I^2 R)$$

Power delivered to the load is

$$P = \frac{(E)^2 R_R}{(R_R + R)^2 + (X_R + X)^2}$$

$$Z = R + jX$$


$$Z_R = R_R + jX_R$$

$$P = \frac{E^2}{4 R_R}$$

Three Phase A.C. circuit

R

or wye (Y) Connected System:-

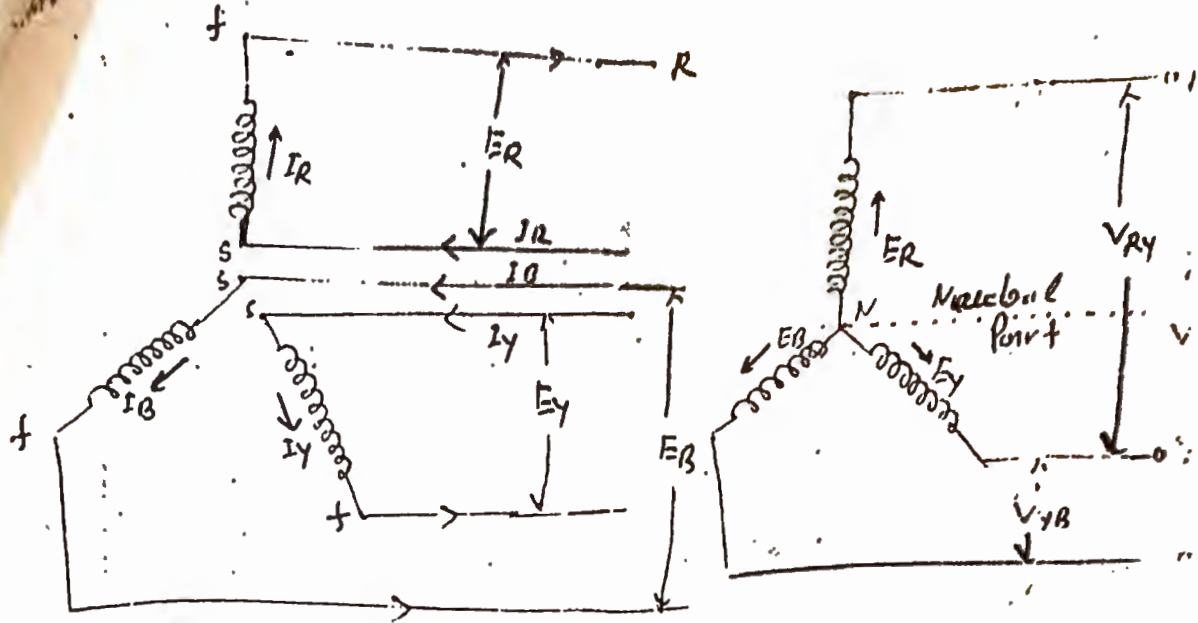

The voltage between any line and the neutral point means voltage across the phase winding is called phase voltage.

The voltage between any two lines is called line voltage. The neutral point is usually earth connected. The positive direction of e.m.f. taken from star point outwards.

Assume $V_R = V_Y = V_B = V_{ph}$

$V_{RY} = V_{YB} = V_{BR} = \text{line voltage } V_L$

$$V_L = \sqrt{3} V_{ph}$$


$$I_L = I_{ph}$$

Total Active Power = $\sqrt{3} V_L I_L \cos \phi$

Reactive " = $\sqrt{3} V_L I_L \sin \phi$

10

... MUST COMPLETE SYSTEM:-

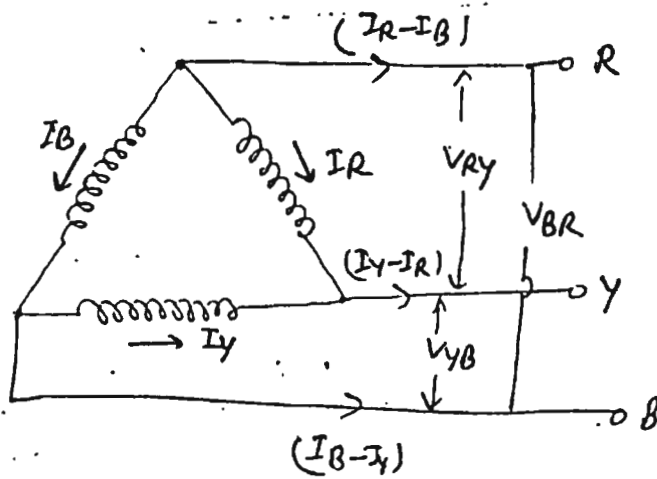

When the starting end of one coil is connected to the finishing end of another coil then Delta connection is obtained

$$V_L = V_{ph}$$

$$I_L = \sqrt{3} I_{ph}$$


Total active Power / Phase

$$= V_p I_p \cos \phi$$


$$\text{Total } P = \sqrt{3} V_L I_L \cos \phi$$

Mohd. Murtaza

Delta Transformation:-

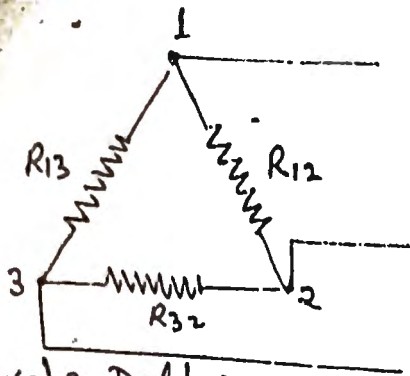

Star to Delta Transformation

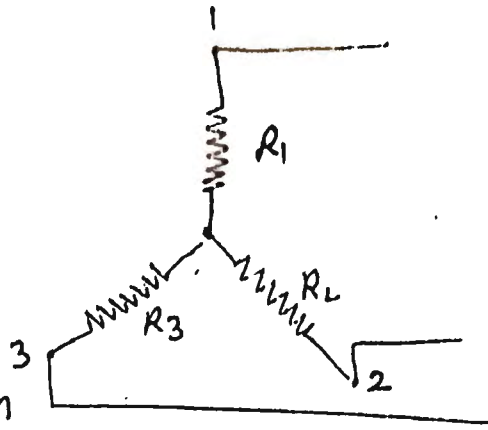

$$R_{12} = R_1 + R_2 + \frac{R_1 R_2}{R_3}$$

$$R_{23} = R_2 + R_3 + \frac{R_2 R_3}{R_1}$$

$R_{13} =$












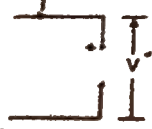


$$R_1 + R_3 + \frac{R_1 R_3}{R_2}$$




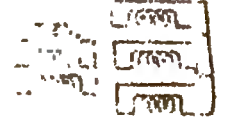






Δ To Star Transformation

$$R_1 = \frac{R_{12} R_{13}}{R_{12} + R_{23} + R_{13}}$$

$$R_2 = \frac{R_{23} R_{12}}{R_{12} + R_{23} + R_{13}}$$

$$R_3 = \frac{R_{13} R_{23}}{R_{12} + R_{23} + R_{13}}$$

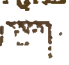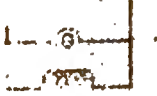8. Open circuit		I is zero for all V
9. Short circuit		V is zero for all I
Quantity	Symbol	
10. Battery		
11. Fixed resistor		
12. Variable resistor		
13. Voltage divider		
14. Inductor		
15. Inductor with iron core		
16. Capacitor		
17. Impedance		
18. Earth		
19. Fuse		
20. Switch contacts (general)		
21. Change-over switch		

23. Lamp or Bulb	
24. Transformer with iron core	
25. Auto-transformer	
26. Three-phase transformer, star-delta connections	
27. DC generator, DC motor	
28. AC generator, AC motor	
29. DC generator, separately excited	
30. DC shunt generator	
31. DC series motor	
32. DC compound motor	

Units of Length, Volume, Mass and Time

Quantity	Unit	Symbol
Length	metre	m
	kilometre	km
	centimetre	cm
Volume	cubic metre	m ³
	cubic centimetre	cm ³